

# Development of TEM High Power RF Vector Modulators

Y. Kang, J. Wilson

M. McCarthy, S-H. Kim, M. Champion, SNS/ORNL

R. Kustom, APS/ANL, B. Chase, FNAL

CWHAP06


May 1-4, 2006

Argonne, IL

OAK RIDGE NATIONAL LABORATORY  
U. S. DEPARTMENT OF ENERGY
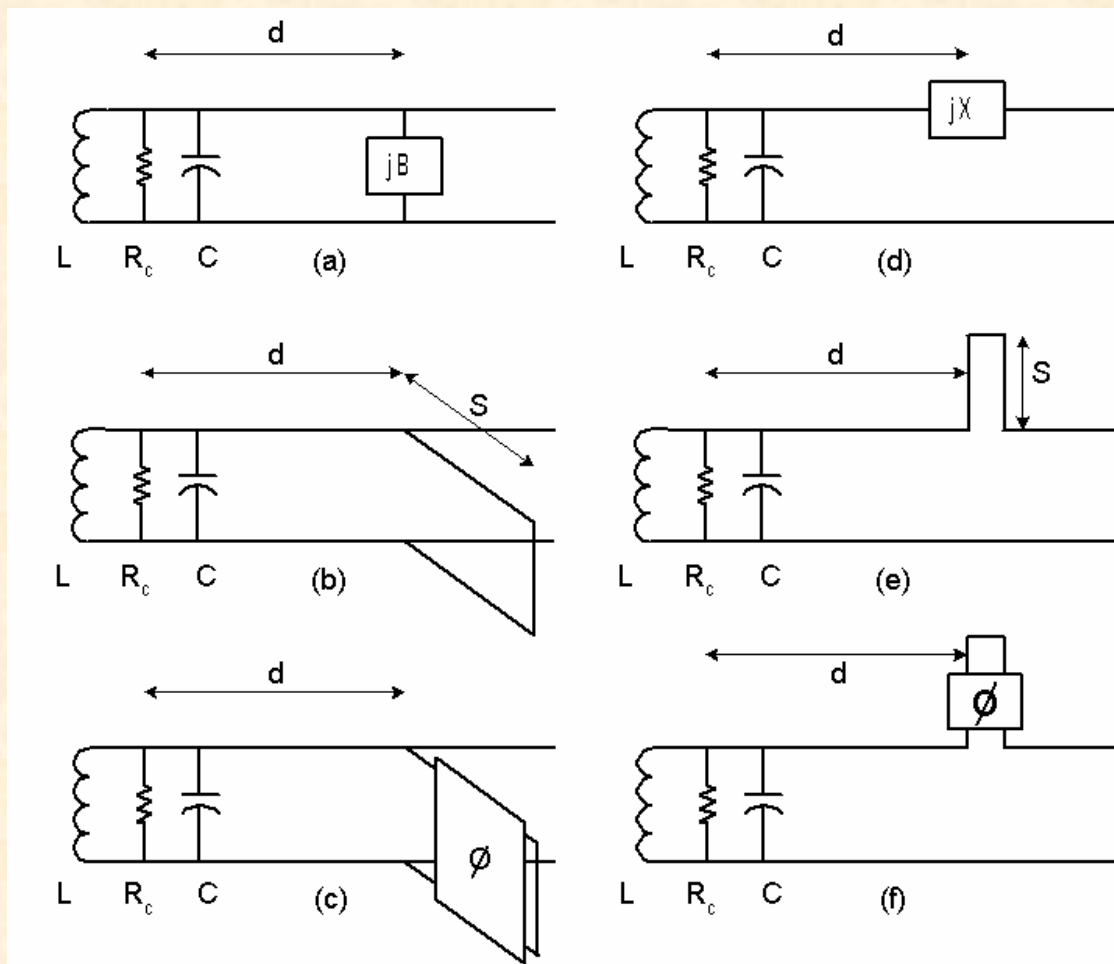
# Cavity Tuning with External Reactance

- Cavity tuning is done externally through RF feed transmission line with at 1 or more adjustable reactances.
  - Using one reactance, the cavity can be matched and tuned at the terminal of the reactance
  - Cavity shunt resistance does not change with the detuning
  - The cavity to the reactance need to be  $N \cdot \lambda/2$



# Tuning, RF Voltage Control


- If the specified amplitude and phase of the voltage in the cavity is delivered, external cavity tuning is already achieved.
- Cavity voltage control is done externally through RF feed transmission line with reactive tuning elements.
- In fan-out RF distribution configuration, having the exact amplitude and phase distributions at cavities gap is important.
- There are advantages and disadvantages to each power splitting scheme, and the splitter itself is an important part of the overall system

# Tuning, RF Control, and Matching

- **The voltage vector control (and tuning) can be achieved using 2 or 3 reactive elements (or short stubs for realization)**
  - 2 stubs may provide sufficient range for the control.
- **For a fixed input voltage resulted by fanning out the klystron output, each cavity port will have a reflected wave**
- **The mutual interaction of the reflections from many cavities must be eliminated**
  - Circulator in each cavity port
  - Use an extra tuning element; no circulator or just one circulator at the klystron output for added protection
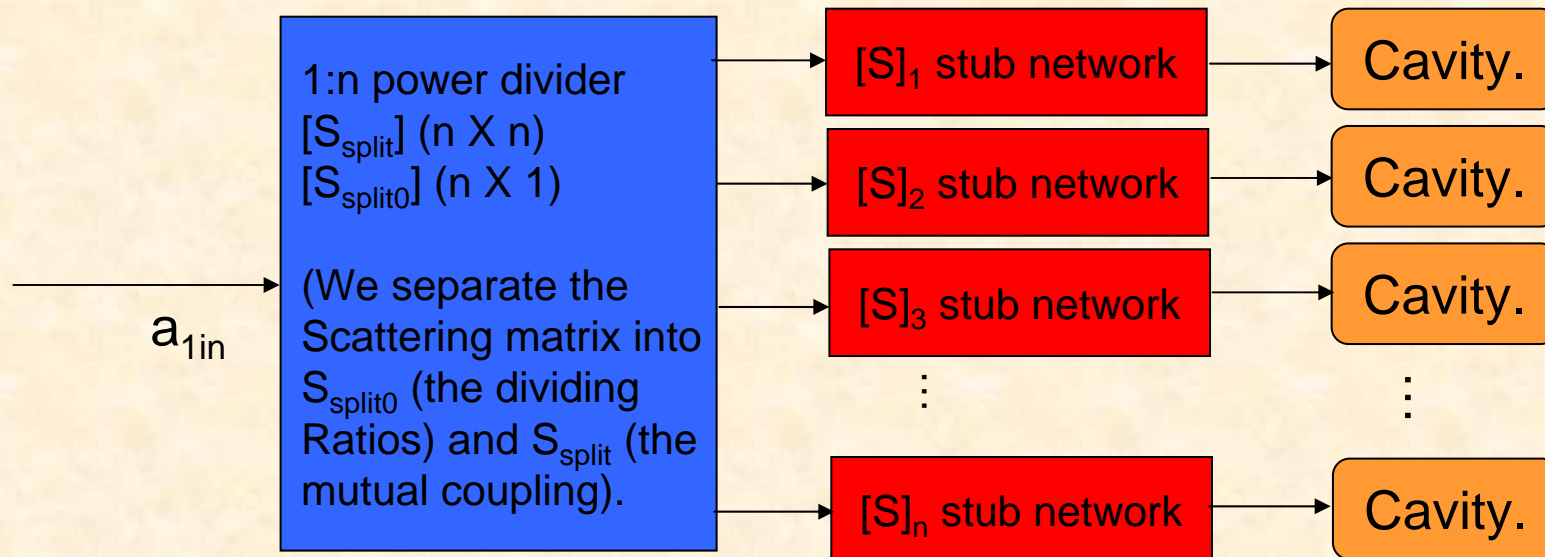
# A Fan-Out Distribution with Stub Tuners

The terminal voltage at the accelerating cavity can be derived as a matrix equation, which must take into account all mutual coupling.



The terminal voltage:  $V_L = Q(1 - S_{split} \Psi)^{-1} S_{split0} a_{1in}$

$$Q_{mn} = \frac{S_{n21} (\Gamma_{Ln} + 1)}{1 - S_{n22} \Gamma_{Ln}} \delta_{mn}$$

$$\Psi_{mn} = \left( S_{n11} + \frac{S_{n12} S_{n21} \Gamma_{Ln}}{1 - S_{n22} \Gamma_{Ln}} \right) \delta_{mn}$$


# A Different Vector Modulator Idea



Quadrature hybrid + 2 half-wavelength tunable slabs

- Advantages:

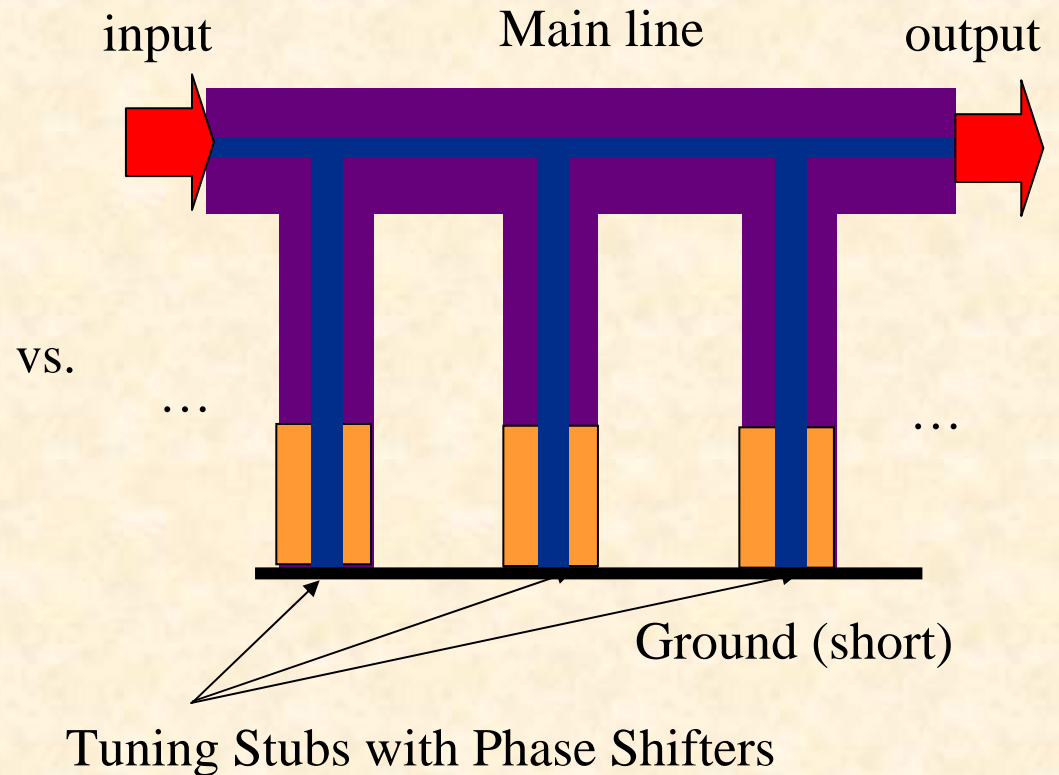- The power can be distributed over a larger volume of tunable material. This leads to easier cooling.
- The need for the hybrid is eliminated.




# Load Terminal Voltages for stub tuners (no loss case)

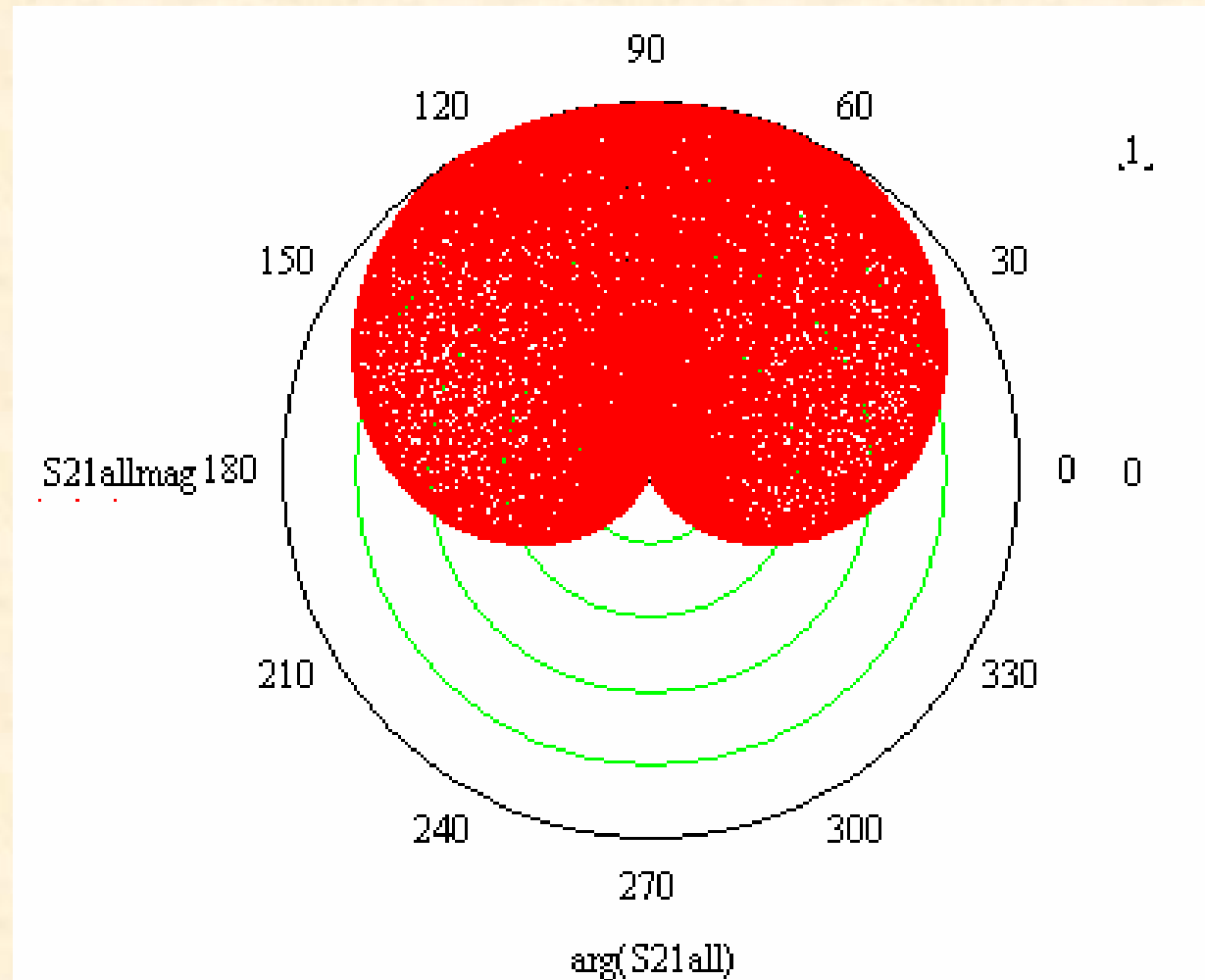0.25  $\lambda$  spacing, 2 stubs from 0 to 0.5  $\lambda$ .  $Z_{\text{stub}}/Z_{\text{line}}=1$

This represents the theoretical MAXIMUM tuning range.


\*Here,  $\Gamma_{\text{load}} = 0$ , so at the terminal  $V_{\text{terminal}} / V_{\text{input}} = S_{21}$



# Load Terminal Voltages for stub tuners (no loss case)

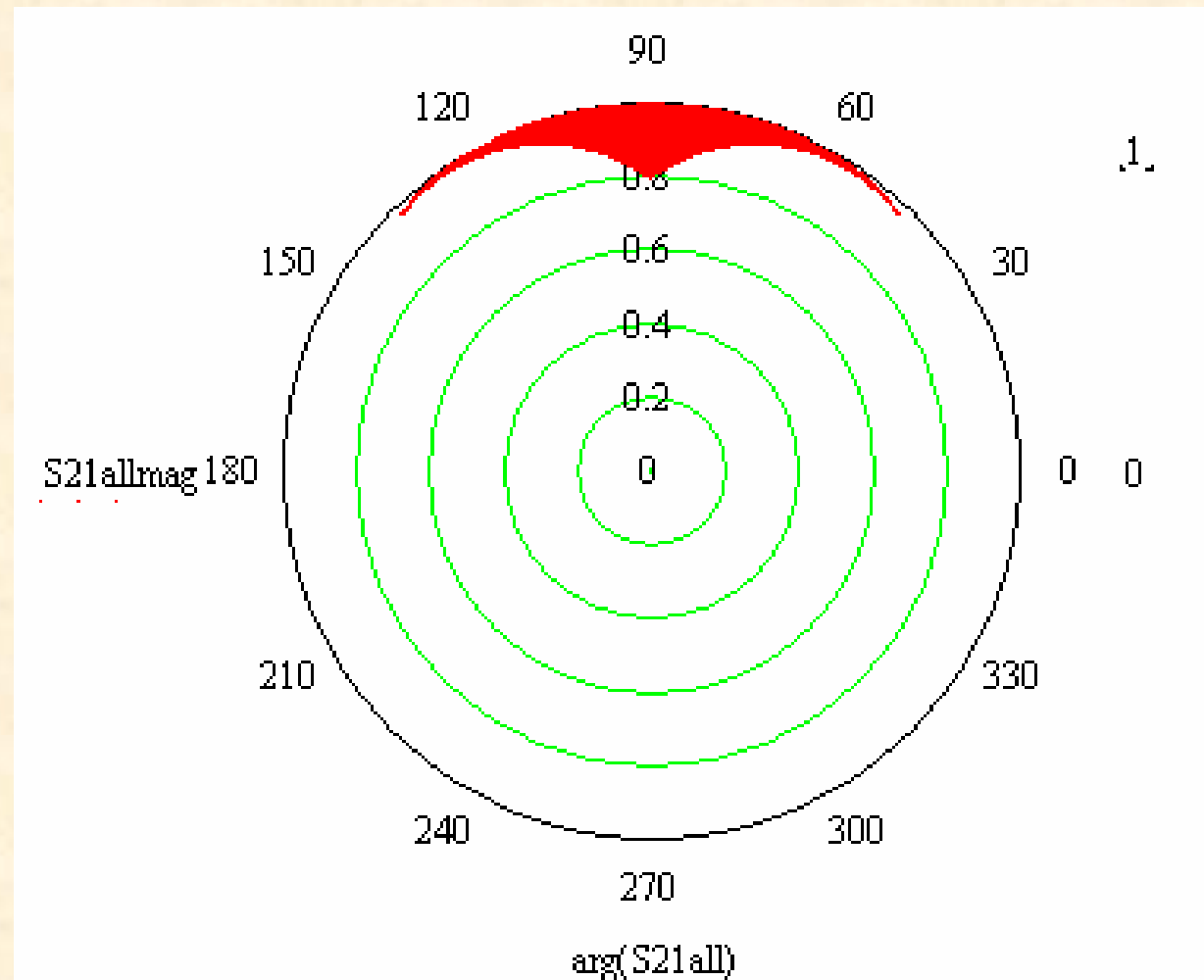0.25  $\lambda$  stub spacing, 2 stubs from 0.15 to 0.35  $\lambda$ .  $Z_{\text{stub}}/Z_{\text{line}}=1$

Since a change in the electrical length of the stub of 0 to 0.5  $\lambda$  is not feasible, we limit our range to 0.15 to 0.35  $\lambda$ .






# Load Terminal Voltages for stub tuners (no loss case)

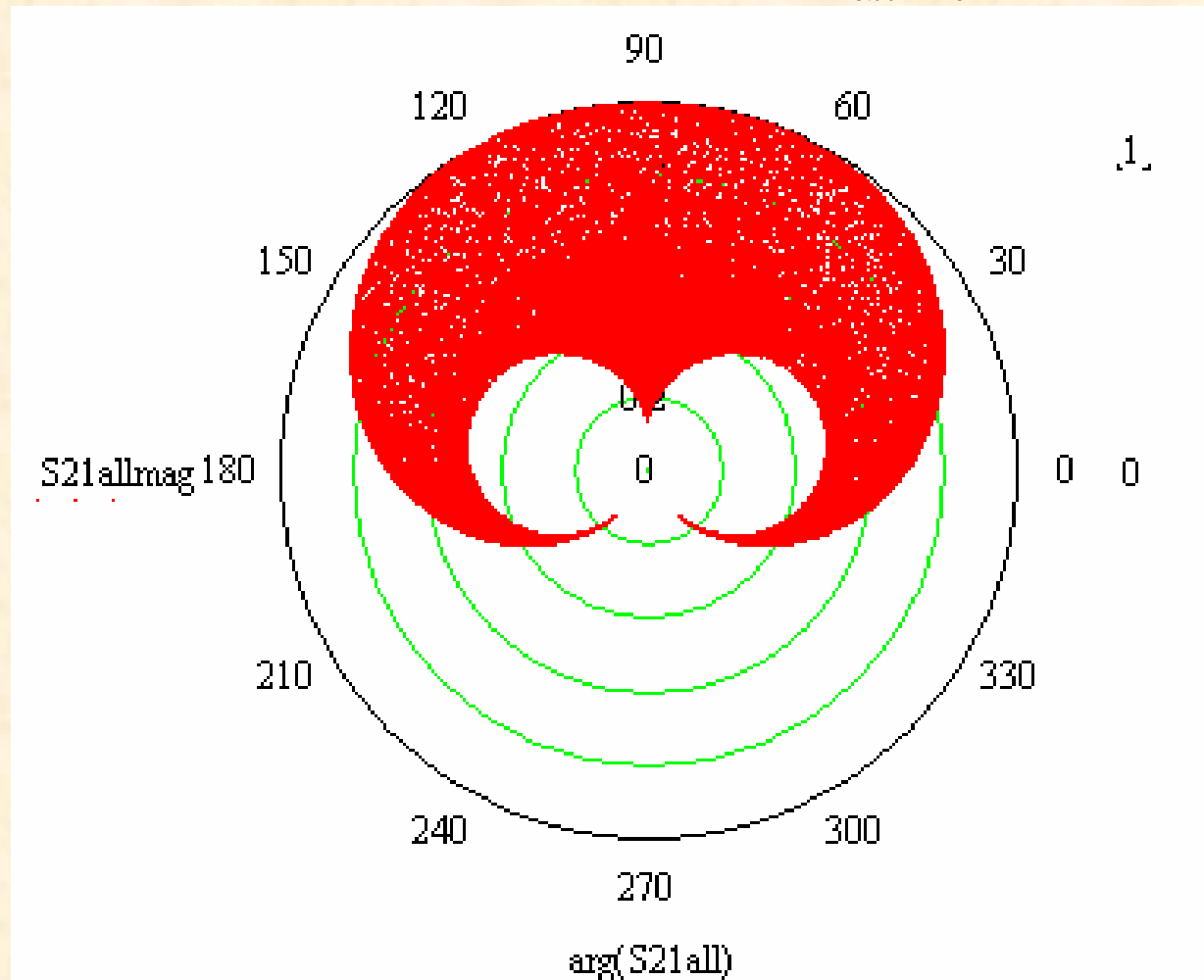0.25  $\lambda$  stub spacing, 2 stubs from 0.15 to 0.35  $\lambda$ .  $Z_{\text{stub}}/Z_{\text{line}}=0.2$


By changing the coupling to the stub (i.e. changing  $Z_{\text{stub}}/Z_{\text{line}}$ ) we can dramatically improve the tuning range.



# Load Terminal Voltages for stub tuners (no loss case)

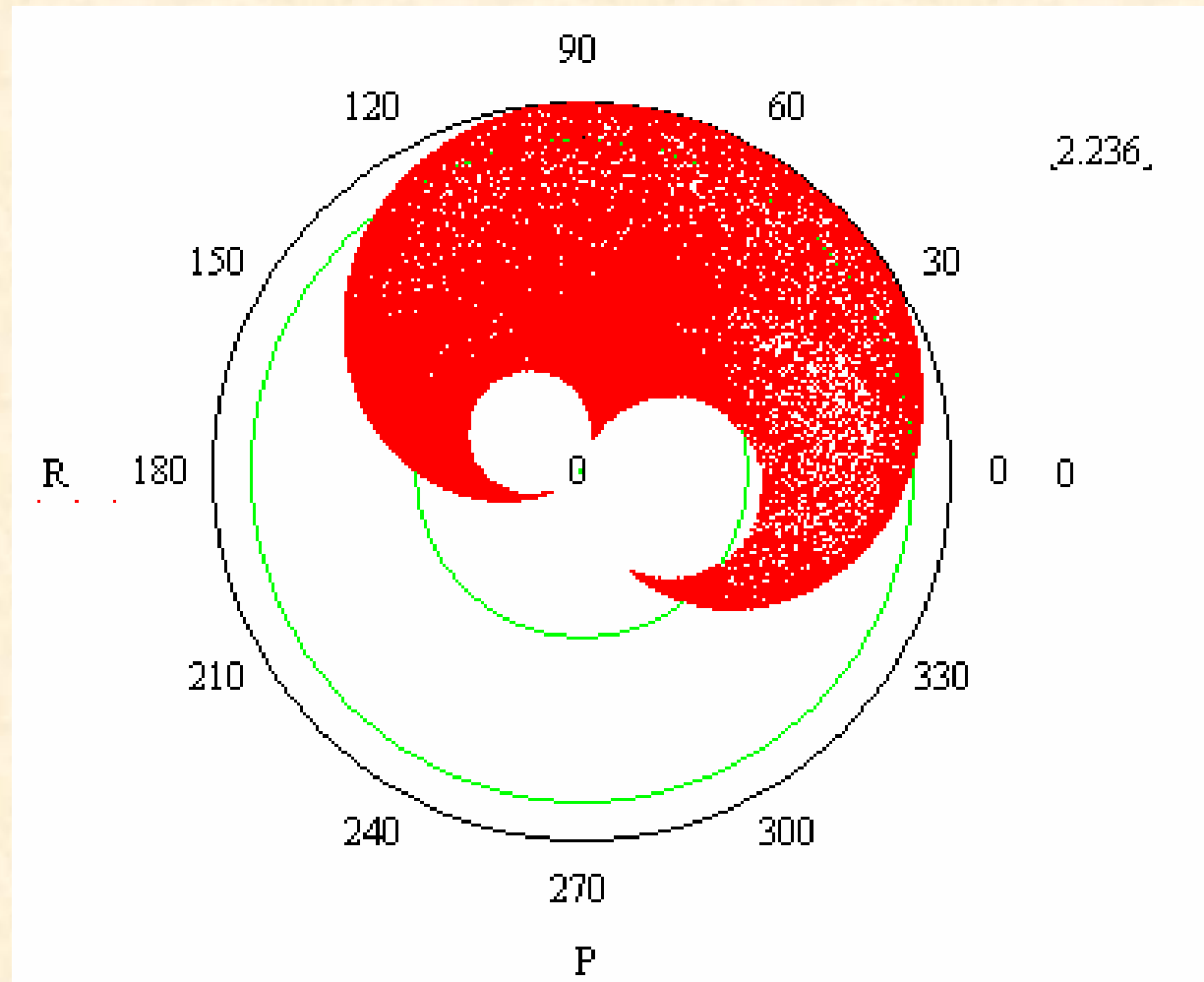0.25  $\lambda$  stub spacing, 2 stubs from 0.15 to 0.35  $\lambda$ .  $Z_{\text{stub}}/Z_{\text{line}}=0.2$


As could be expected, changing Gamma, load to  $0.5+j0.5$  will shift the tuning range slightly, as shown.



# Load Terminal Voltages for stub tuners (no loss case)

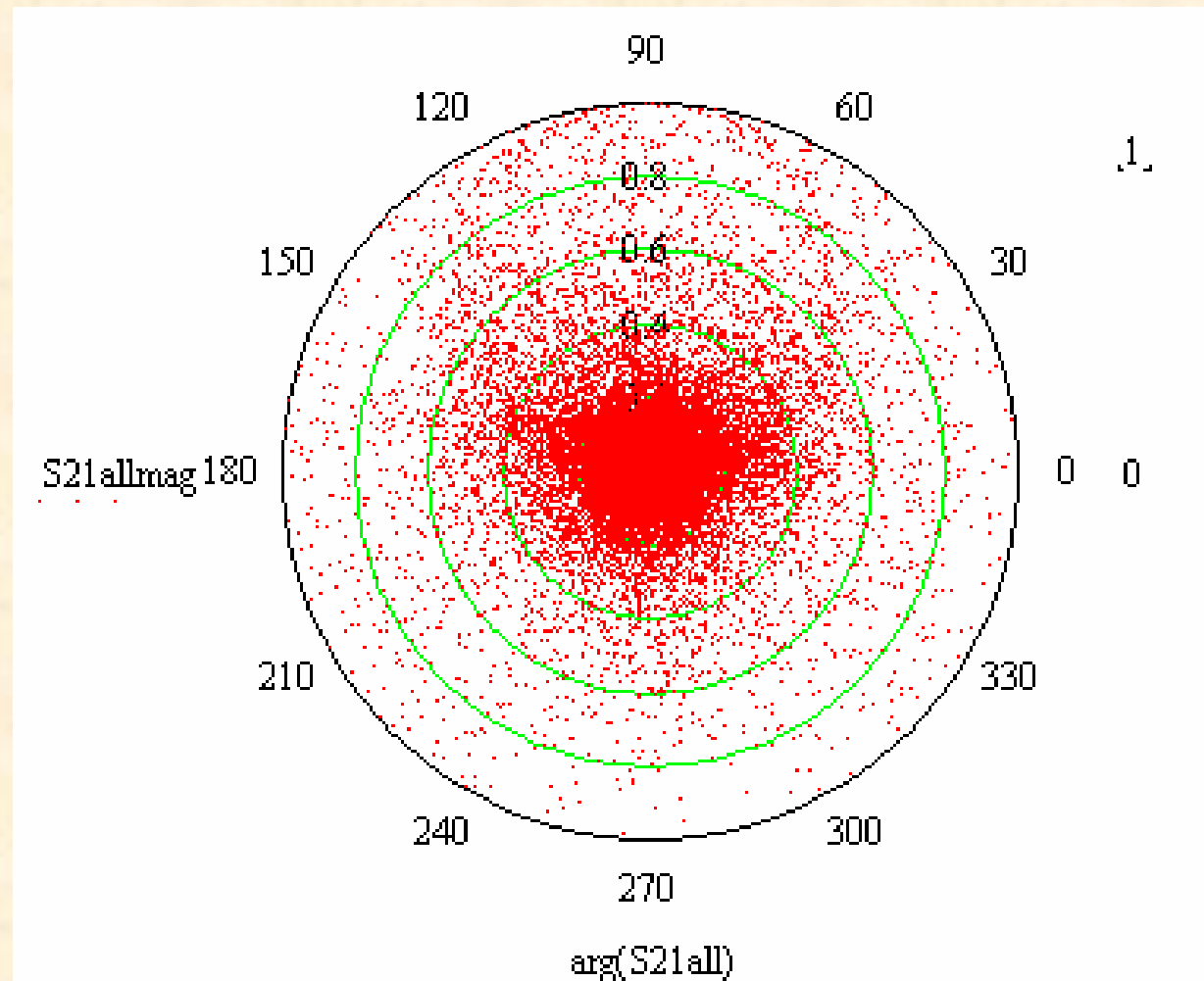
0.25  $\lambda$  stub spacing, 3 stubs from 1 to 0.5  $\lambda$ .  $Z_{\text{stub}}/Z_{\text{line}}=0.2$

Using 3 stubs can provide FULL vector control. However, this is not typically required in accelerator applications.



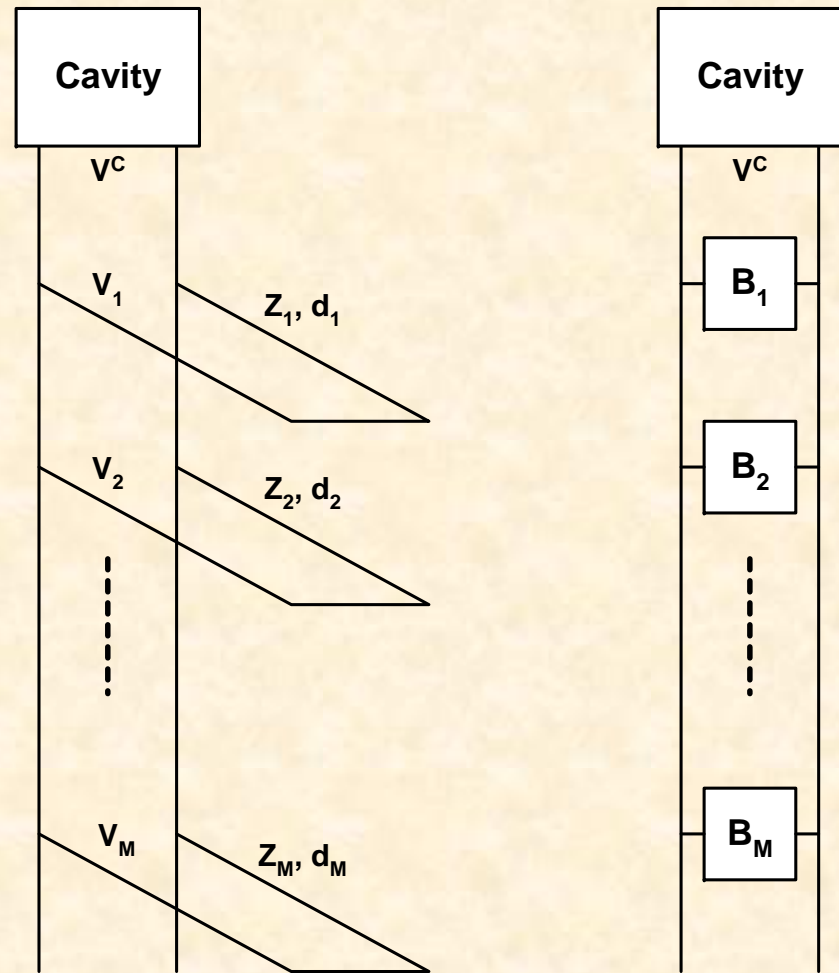
# Applying RF Voltage to a Cavity

- The cavity can have a specified voltage using two or more reactances in the feed transmission line
- The reactances are realized with short circuited transmission line sections
- Two tuning elements can deliver a limited range of voltage vector control
- Three tuning elements can deliver full range of voltage vector control



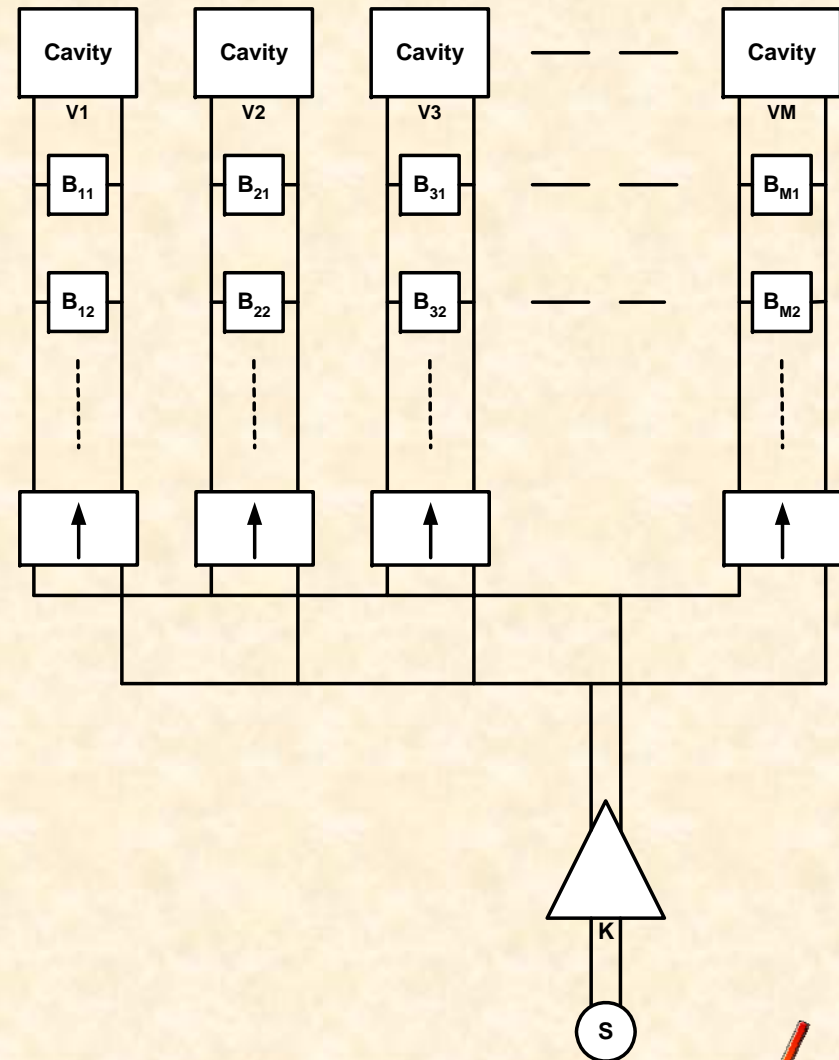
# Determining Reactive Elements for Fan-Out Multicavity Operation

- Cavities are driven through transmission line stub networks
- For a specified set of voltage vectors, each stub network will have reflected power
- Each splitter output must be protected with an isolator (or a circulator), since the mutual interaction can cause disruptions in the voltage vector control
- Additional reactances at the splitter ports may tune out the reflection at the klystron amplifier output
- The reactances can be found setting up a system admittance matrix



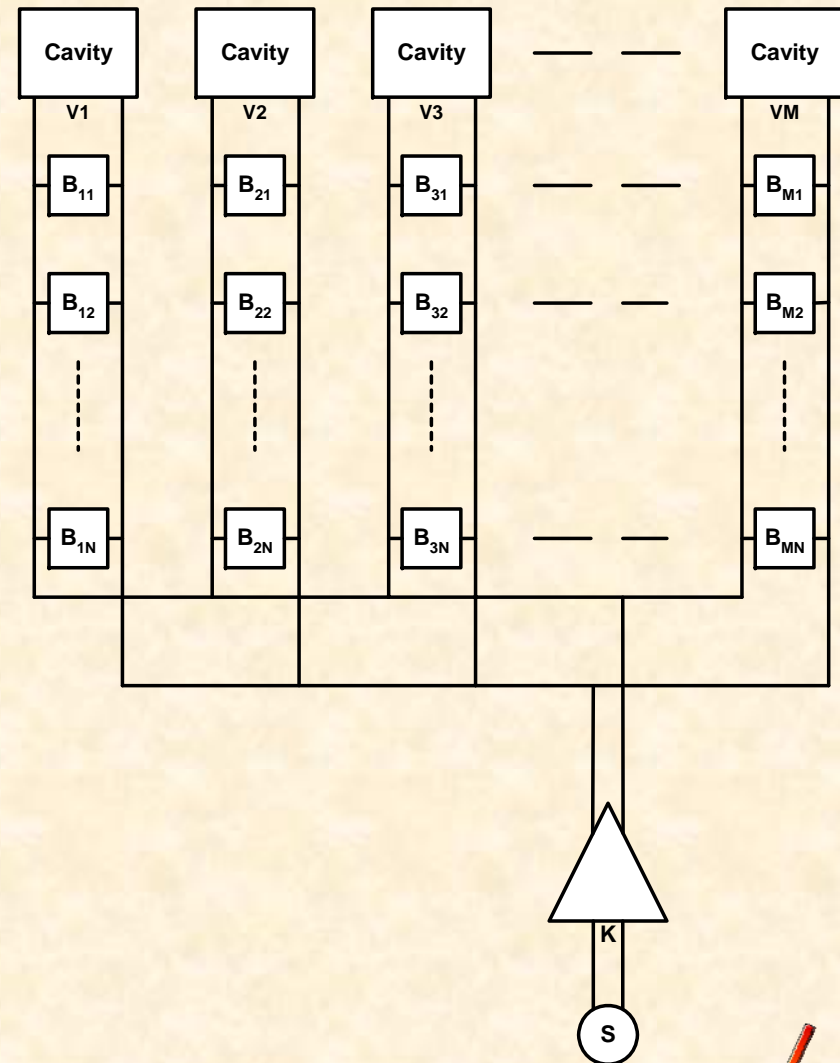
# Determining Reactive Elements for Fan-Out Multicavity Operation

- Reactive tuning is done at each splitter output port
- Additional reactances at the splitter ports may tune out the reflection at the klystron amplifier output
- The reactances can be found setting up a system admittance matrix




# The Vector Modulation Using Hybrid Junction

- **Transmissive**

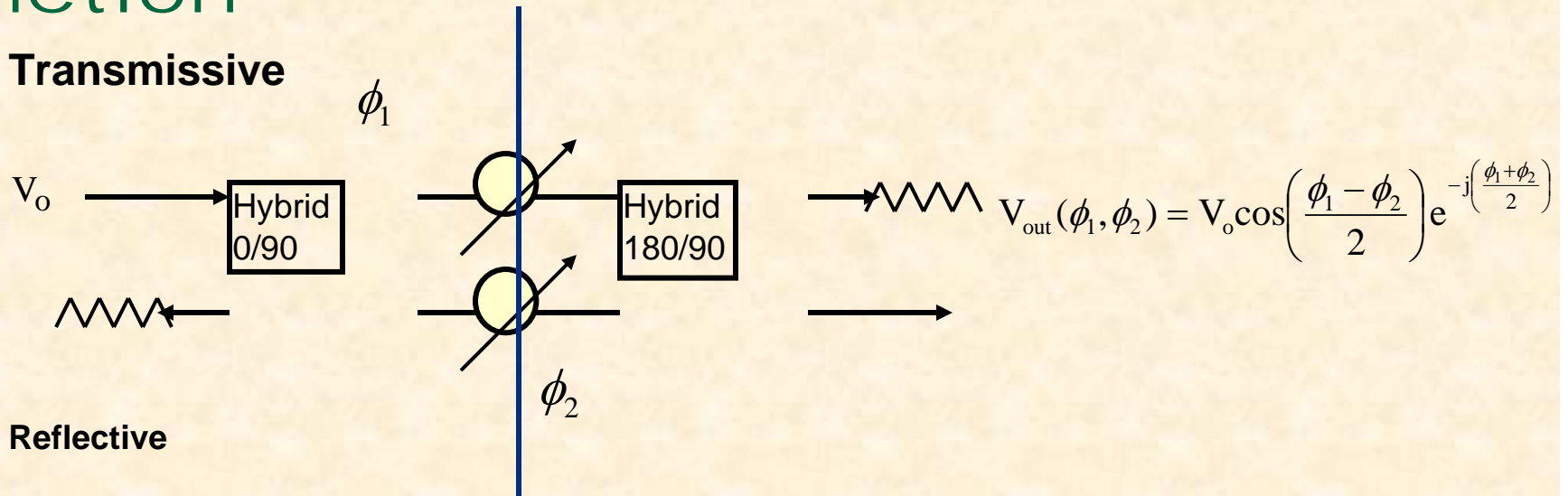


- **Reflective**

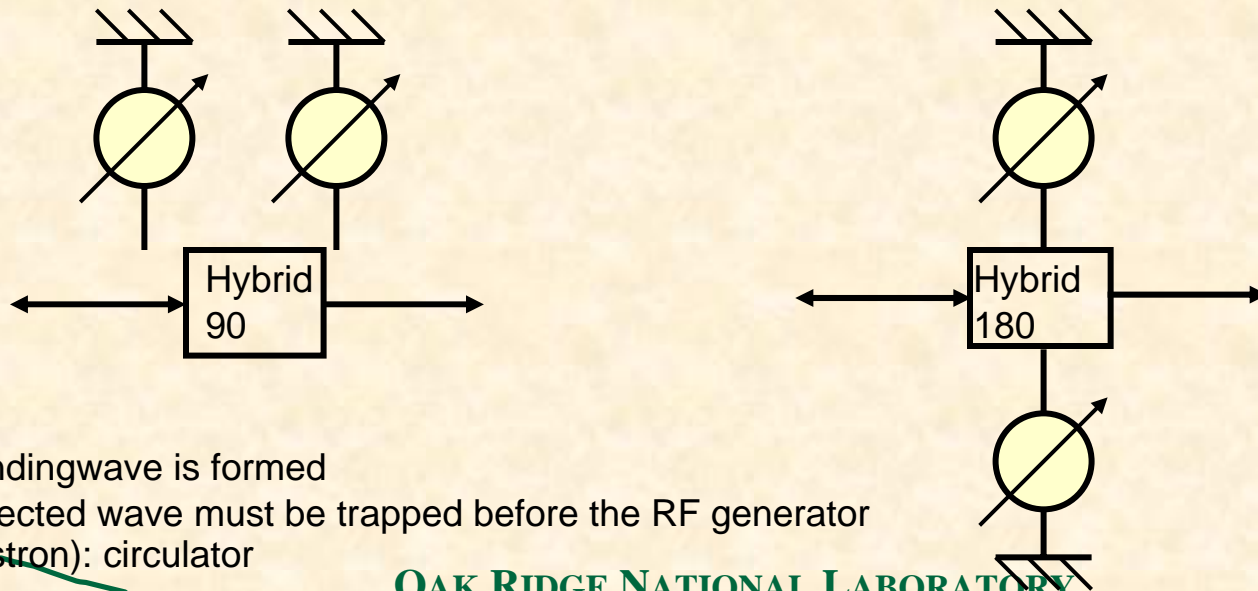

- Standingwave is formed
- Reflected wave must be trapped before the RF generator (klystron): circulator
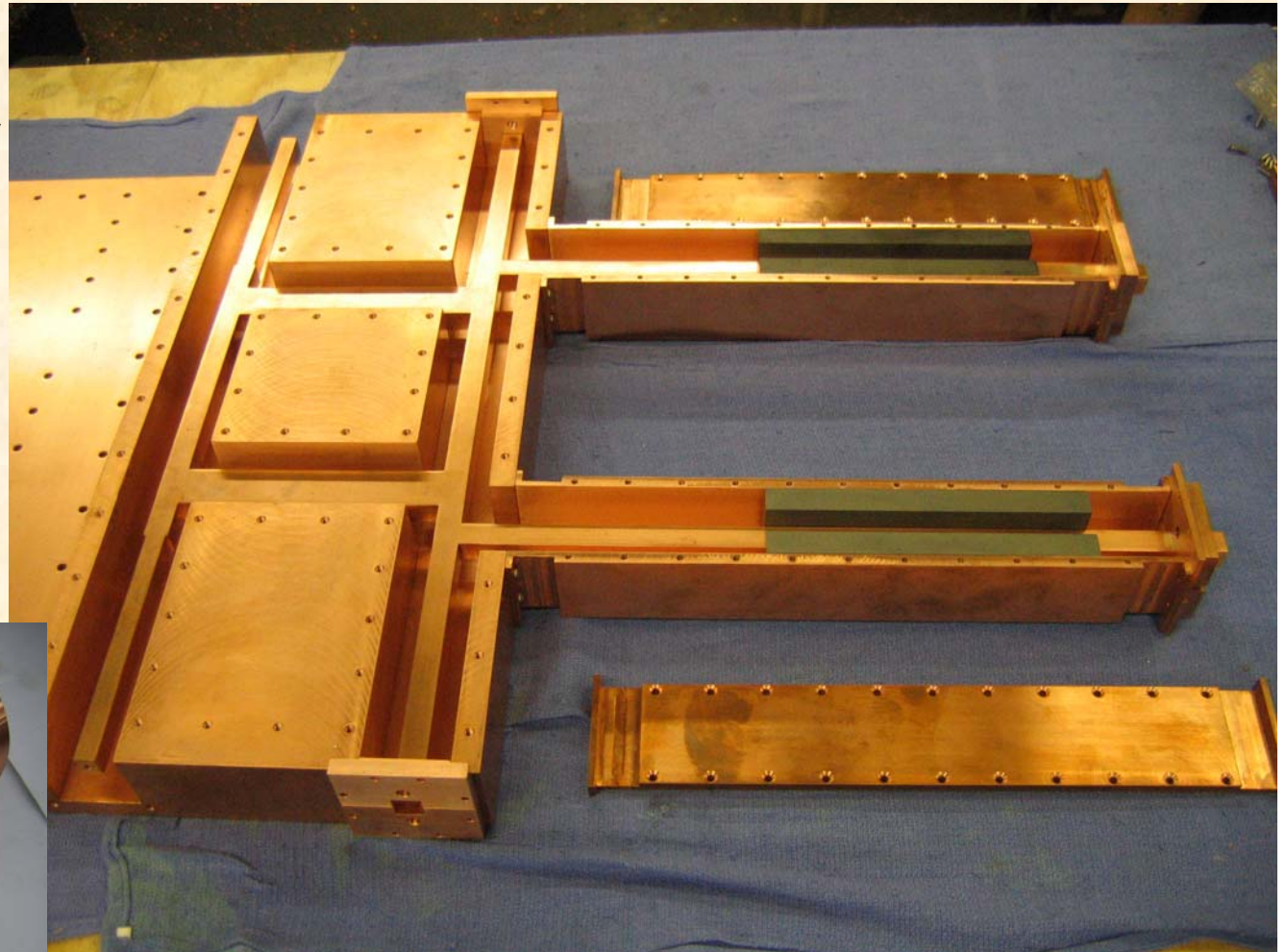
# Prototype Vector Modulator



- Manufacturing parts completed and assembling is under way
- Center conductor is supported by two  $\lambda/4$  stubs for cooling
- RF testing to be performed





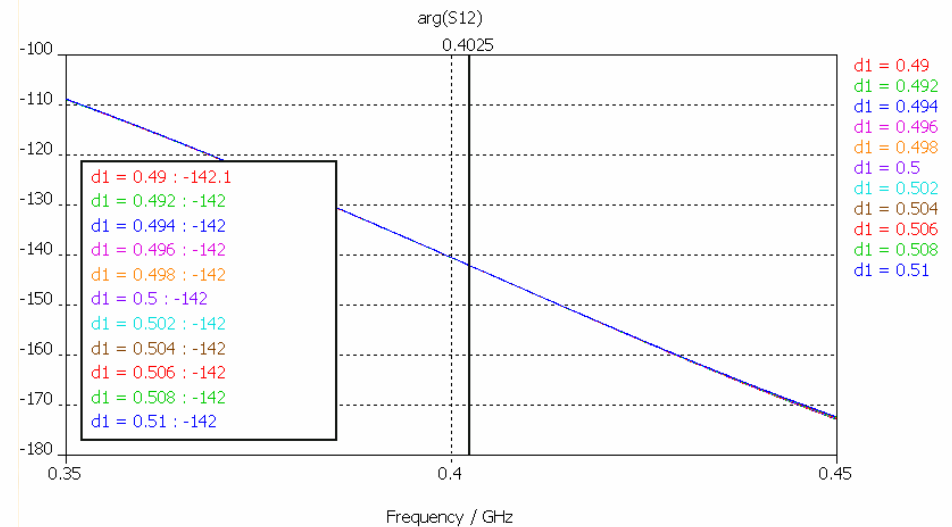
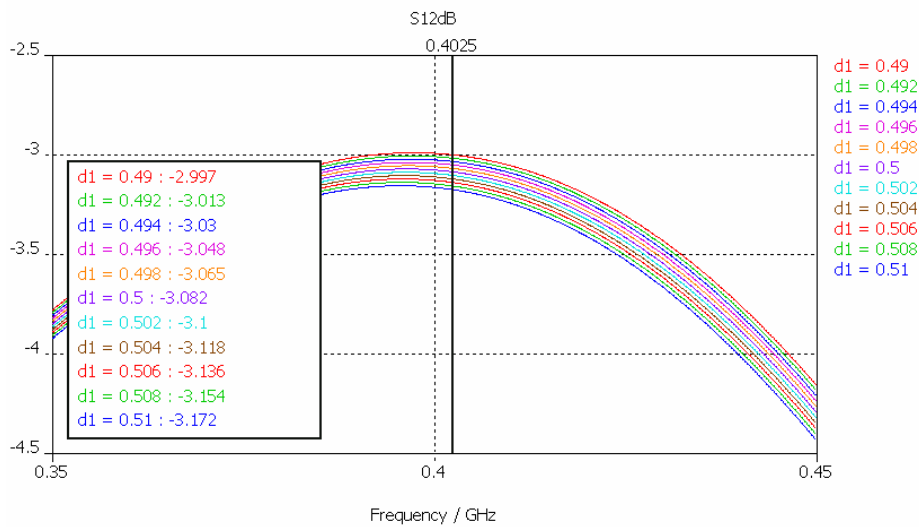
# Square coax dimensional Sensitivity Hybrid Junction (50Ω section)

- 50Ω section center conductor width ranging from 0.49...0.51 inches



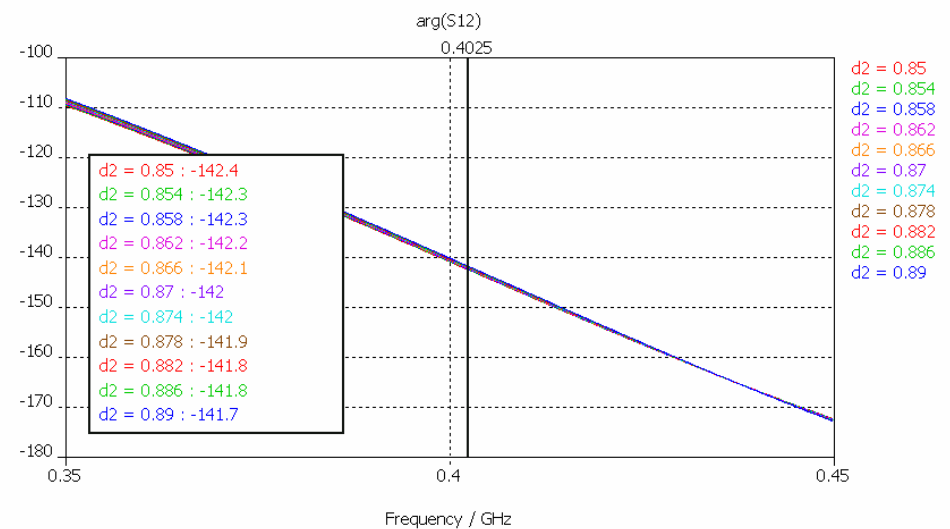
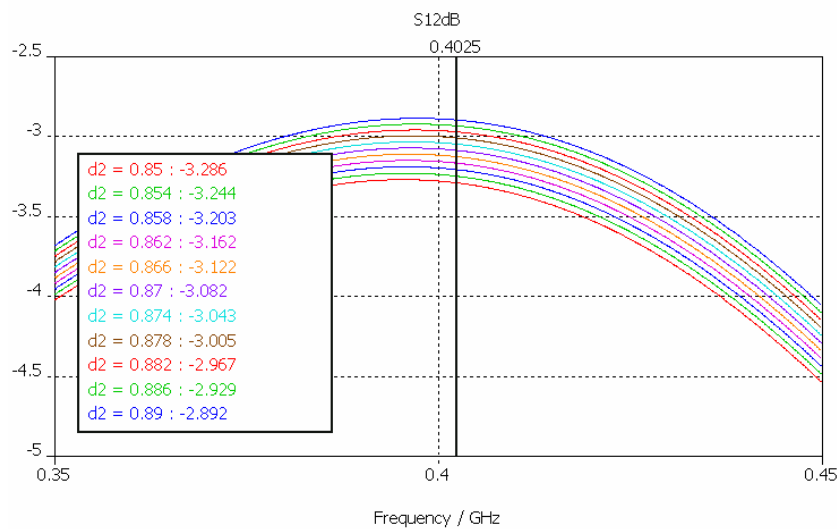
# Square coax dimensional Sensitivity Hybrid Junction (50Ω section)

- 35Ω section center conductor width ranging from 0.85...0.89 inches


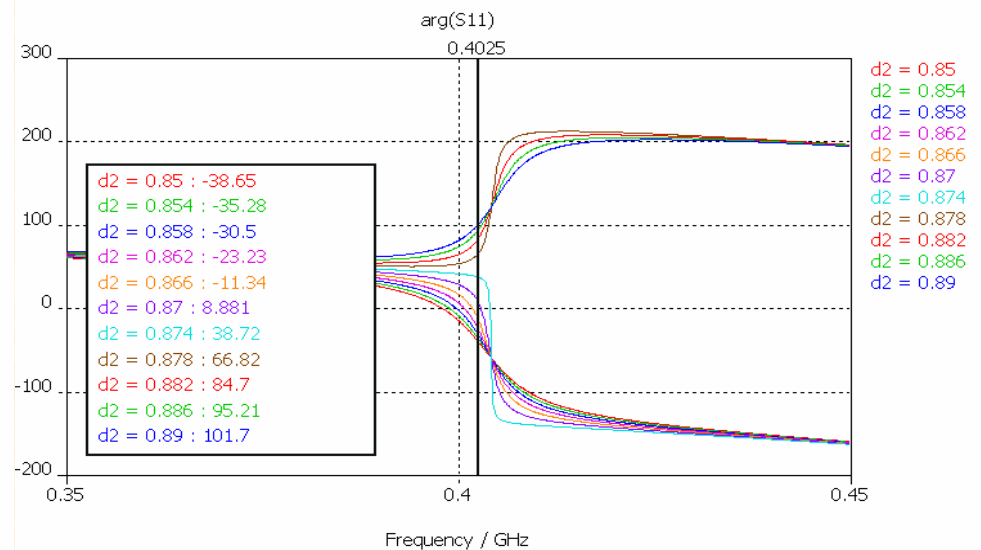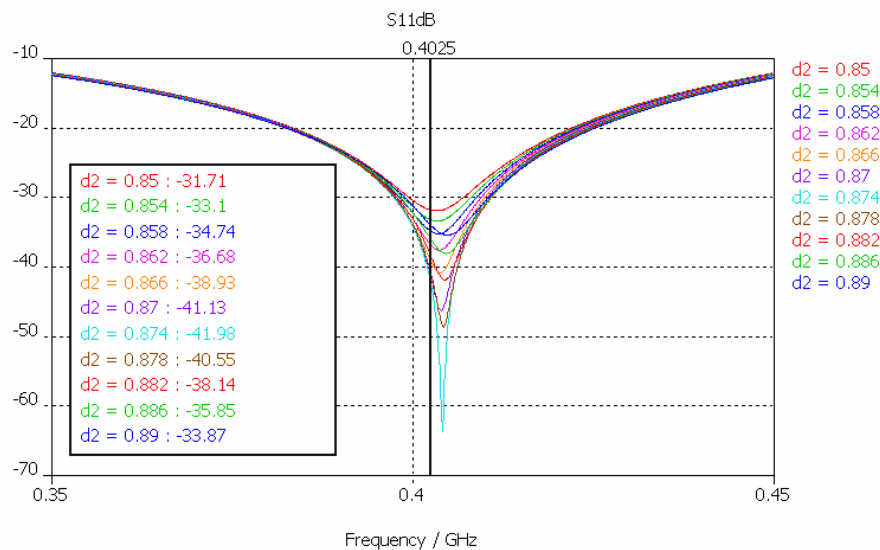
# Square coax dimensional Sensitivity Hybrid Junction (50Ω section)

- 35Ω section center conductor width ranging from 0.85...0.89 inches



# Ferroelectric materials

Ferroelectrics can be tuned with an external *electric* field

The relationship between the electric field and flux density can be approximated (in the lossless case) by

$$E = \alpha D + \beta D^3$$

where  $\alpha$  and  $\beta$  are functions of temperature.

The definition of (ac) permittivity, then, is

$$\epsilon' = \frac{dD}{dE}$$

For small ac signals, this quantity can be approximated by a constant, and the system behaves linearly.

*Shepard Roberts, "Dielectric and Piezoelectric Properties of barium titanate," Phys. Rev. 71, 890 (1947).*

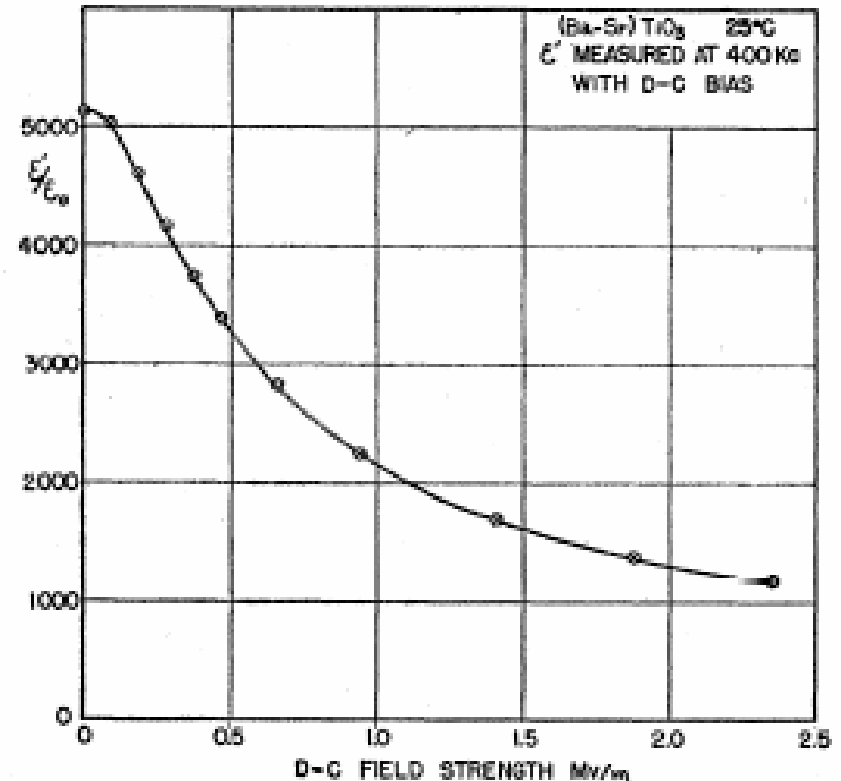



FIG. 4. Dielectric constant of (Ba-Sr)TiO<sub>3</sub> versus d.c. field strength.

**\*New ferroelectric materials have been developed recently with excellent microwave properties**

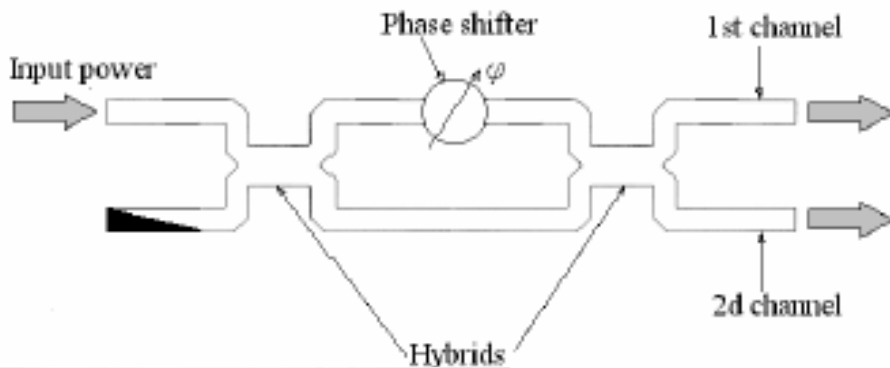
# A look at previous research

We would like to explore a structure that could also be used at lower frequencies.

- Frequency: 11.424 GHz (X-Band)
- >96% efficient at 250 MW
- 200 degree phase shift, 100kV bias
- Uses 4 partially filled resonant cavities placed a quarter-wavelength apart.
- Cavities are partially loaded with BST ceramic.



Architecture of RF switch

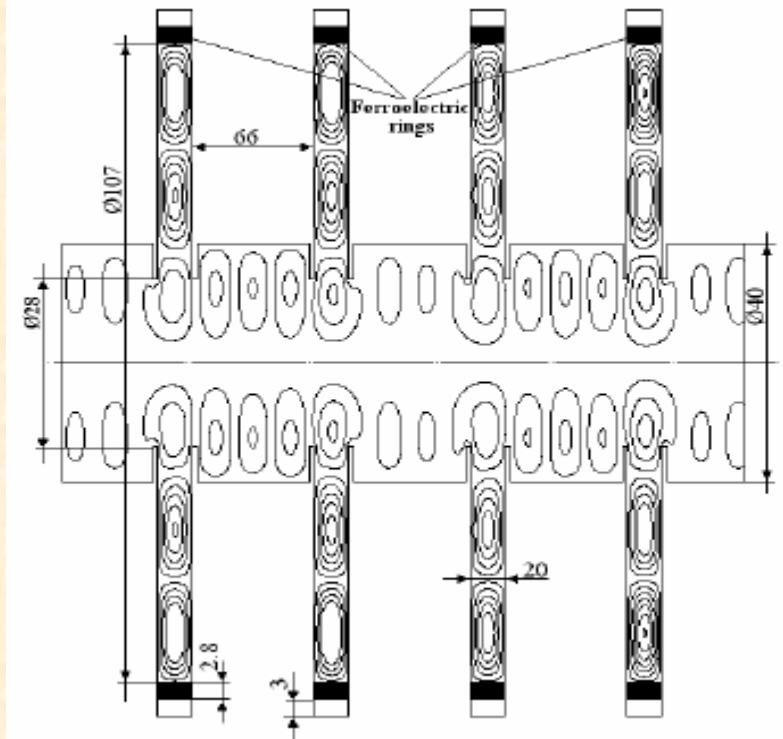

BST Ceramic  
 OD: 34 mm  
 ID: 20 mm  
 Thickness: 8mm

*V.P. Yakovlev, O.A. Nezhevenko, and J.L. Hirshfield  
 11<sup>th</sup> Advanced Accelerator Concepts Workshop 2004.*




**OAK RIDGE NATIONAL LABORATORY**  
**U. S. DEPARTMENT OF ENERGY**


DOE Semi-annual Review, May 2-3, 2006




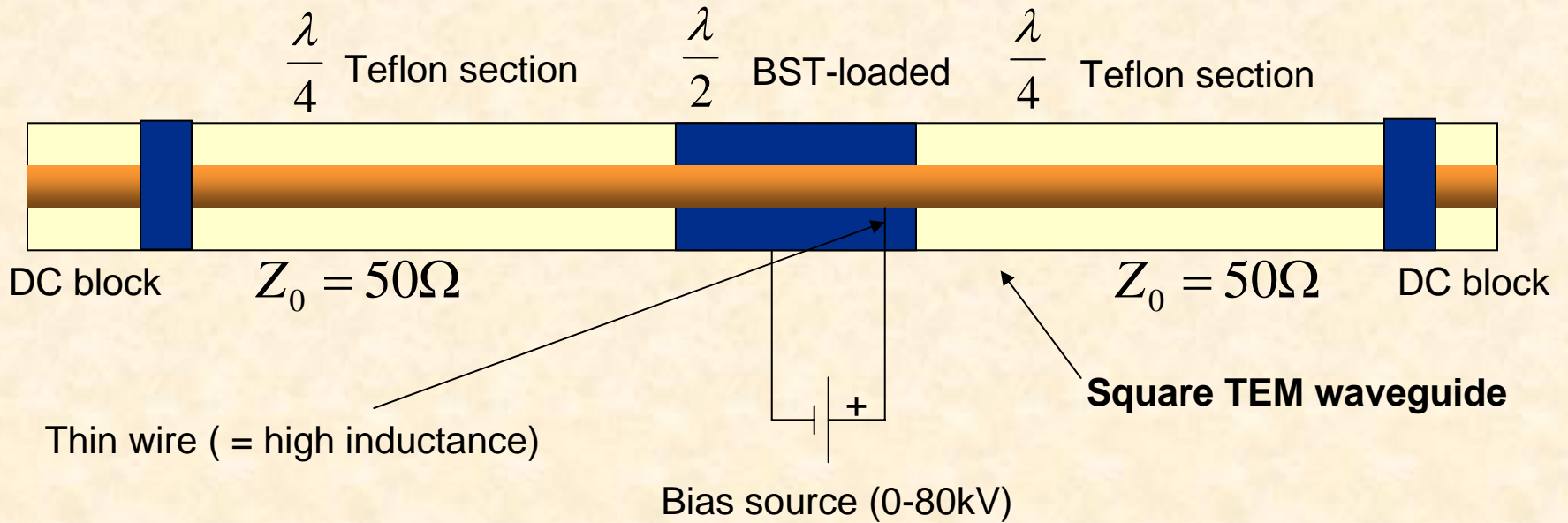
# New Ferroelectric Phase Shifter – Test Structure



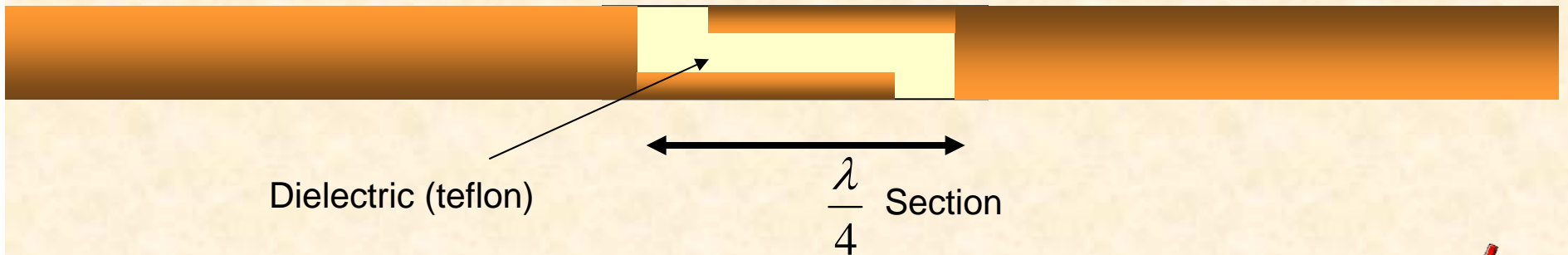Coupled line DC block – also acts like 402.5 MHz filter!



# Ferroelectric Phase Shifter Structure

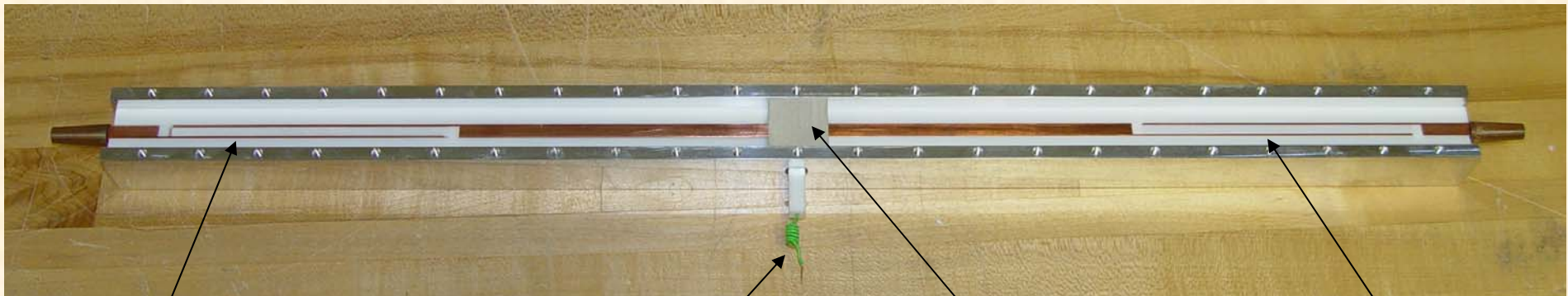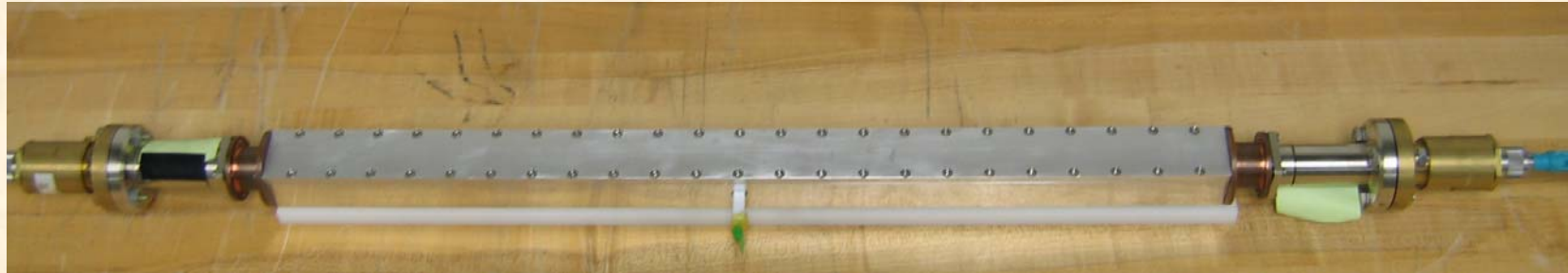

DC block

DC bias feed

BST

DC block

- \* A small 6 degree phase shift has been measured with a 2 kV biasing potential.
- \* An alumina matching section is being developed to improve performance by lowering insertion loss.


# SNS RF Test Facility (RFTF)

- The prototype VM will be tested in the SNS RFTF
- RFTF has been used for various cavity power coupler RF conditioning
  - SNS SRF couplers were conditioned using a 550 kW, 805 MHz klystron
  - Presently a 5 MW klystron is being used for BNL SRF photoinjector couplers
- The two klystrons have been installed completely – April, 2006
  - 402.5 MHz, 2.5 MW peak, 1.3 msec, 8% DC
  - 805 MHz, 5 MW peak, 1.3 msec, 8% DC
- HV Converter Modulator
  - 10 MW capacity that can drive the SNS klystrons
- RFTF
  - The existing building is being reconfigured
  - Test cave is being equipped
- SRF facility
  - An additional SRF building is under construction – completion by Sep. 2007
  - Vertical and horizontal testing of SRF structures and more


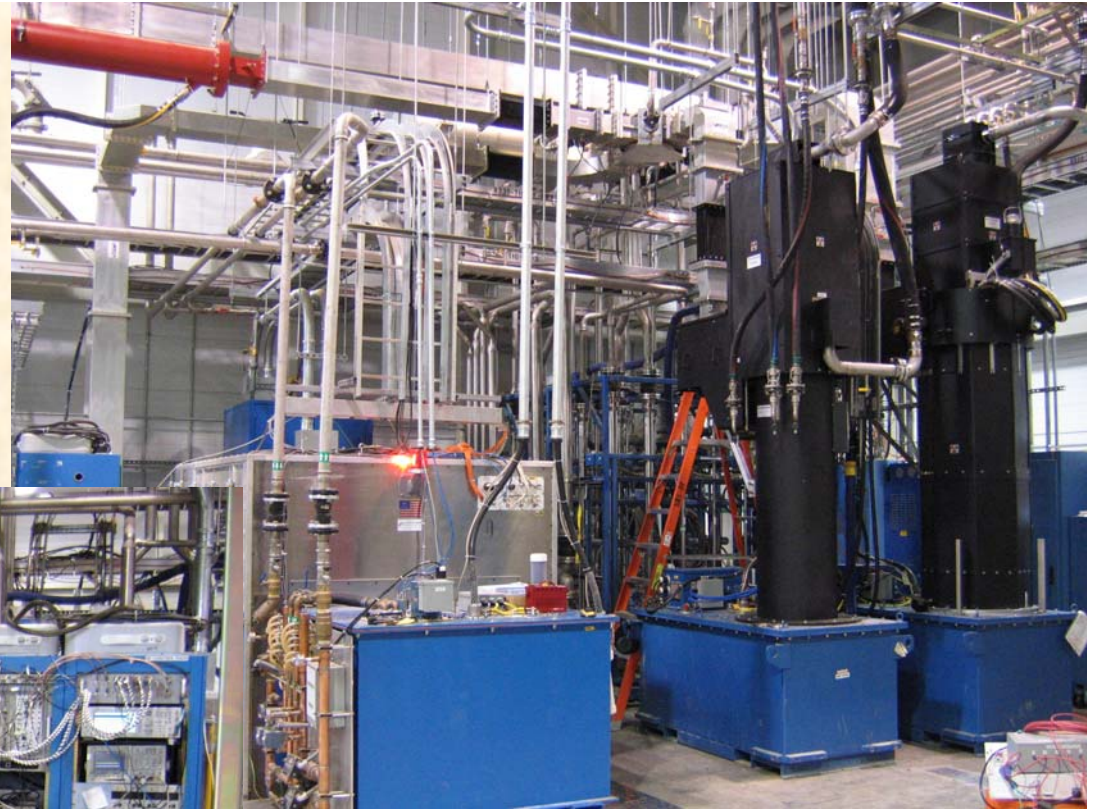
# RFTF

- Two klystrons installed and tested (402 MHz and 805 MHz)



- Coaxial couplers under RF processing (805 MHz)

# Summary

- RF vector modulation and tuning methods
  - For fan-out RF power distribution
  - Elimination of circulators
- Development of phase shifters
  - Ferrite phase shifter
  - Ferroelectric phase shifter
- Prototype vector modulator being built
  - Hybrid coupled design
  - High power RF testing to be performed
  - Will demonstrate the ferrite phase shifter performance