



# **Modern and Crowbarless HVPS**



W. Tron, RF power amplifier

Paul Scherrer Institut, 5232 Villigen-PSI, Switzerland

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron



# **Table of Contents**

- 1) History of PSM
- 2) Pulse Step Modulation Technology
- 3) PSM for Scientific Applications
- 4) PSM @ PSI





# **History of PSM**



Paul Scherrer Institut, 5232 Villigen-PSI, Switzerland

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron





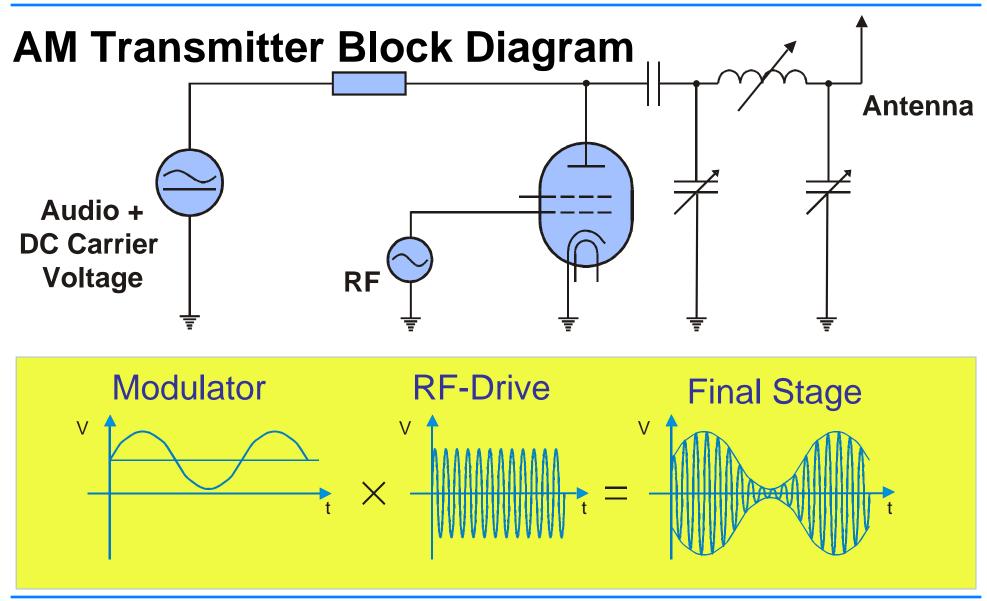
# **PSM Technological Development**

- AM-Transmitter Basic Technology
- B-Modulator Design (Linear System)
- 'Modern' Switched-Mode Systems
  - PDM Modulator
  - Pulse Step Modulator







Paul Scherrer Institut, 5232 Villigen-PSI, Switzerland

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron







# **Typical Modulator Specification**

- DC-Voltage 14 kV (Carrier Voltage U<sub>C</sub>)
- Superimposed audio modulation resulting in output voltage range 0 .. 28 kV
- Continuous output power 1 MW, peak power 2.5 MW
- AF-bandwidth 50 7500 Hz
- Signal-to-Noise-Ratio better than 60 dB
- Total Harmonic Distortion < 3 % (THD incl. RF-Part)
- High efficiency > 97 %



# **PDM Modulator**

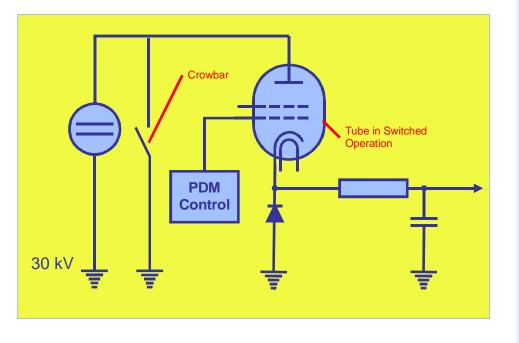

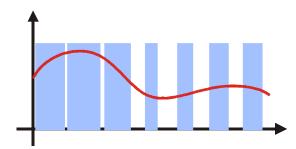


Switched mode operation
 Improved efficiency

#### **BUT**:

- Tube cathode on high voltage
  - Difficult to control
- Requires very fast high voltage diode
  - Series Connection of Diodes
  - Problems with Stray Inductance
- High switching frequency necessary
   > 50 kHz
- Output filter network
  - High damping on switching frequency required
- Crowbar system needed


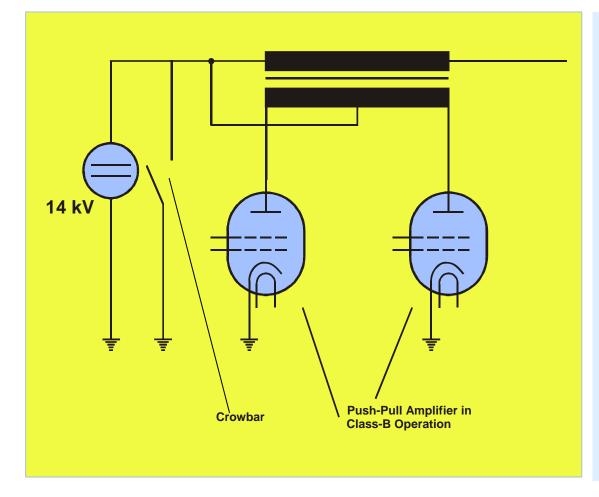
# **Linear Tube Modulator in Class-B Operation**



- Requires tubes for operation

   Expensive devices with limited lifetime
   Ligh basting power
  - High heating power
- Tubes in Class-B operation

   Low Efficiency (Linear Operation)
- Carrier voltage from DCsource
  - Carrier voltage fixed
  - High stored energy, therefore
    - crowbar system needed





# **PSM Technology**






# The Pulse Step Modulation

- Introduced by Thomson & Multimedia, Switzerland (formerly BBC / ABB) in 1983
  - Invention keyed by restrictive licensing policy of PDM competition
- Since 1983 continuous improvements of the system
  - IGBT (Insulated Gate Bipolar Transistors) instead of GTO (Gate-turn-off-Thyristor) as switching device
  - Fast Feedforward Regulation
  - Increase in bandwidth from 4.5 kHz to 50 kHz




# **PSM Block Diagram**

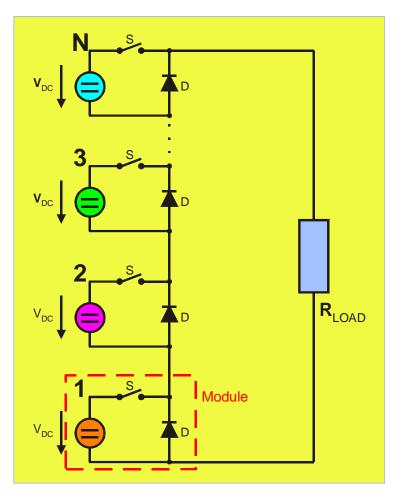

- The system consists of N seriesconnected switched mode power supply modules
- Each module consisting of
  - DC voltage source V<sub>DC</sub>
  - Switching Element S
  - Free-Wheeling Diode D
- The voltage  $V_{DC}$  is equal on all modules
- With switch S the voltage V<sub>DC</sub> can be switched to the output
- If switch S is open, the diode D provides a current path for the output current




# **Coarse Step Modulation (CSM)**

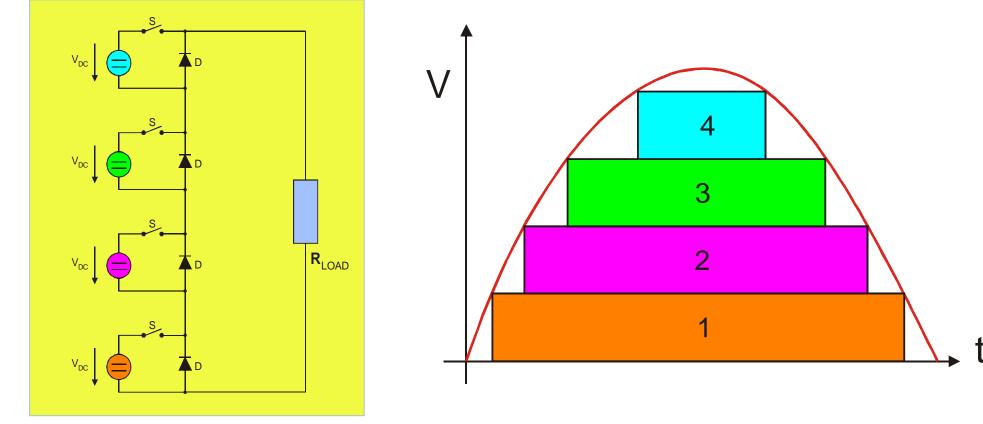

The output voltage can be controlled stepwise to achieve the required level




# **Coarse Step Modulation (CSM)**

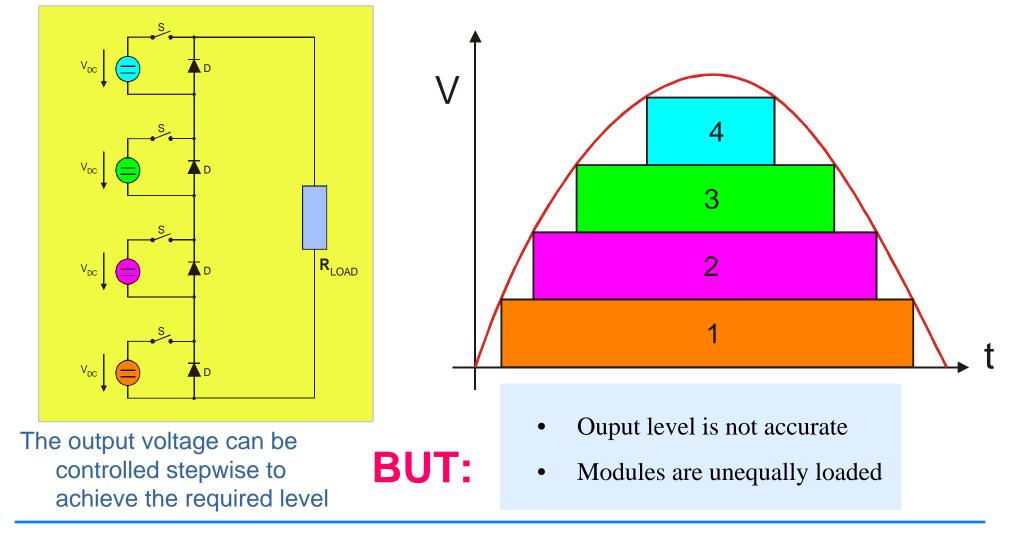






# **Pulse Width Modulation (PWM)**

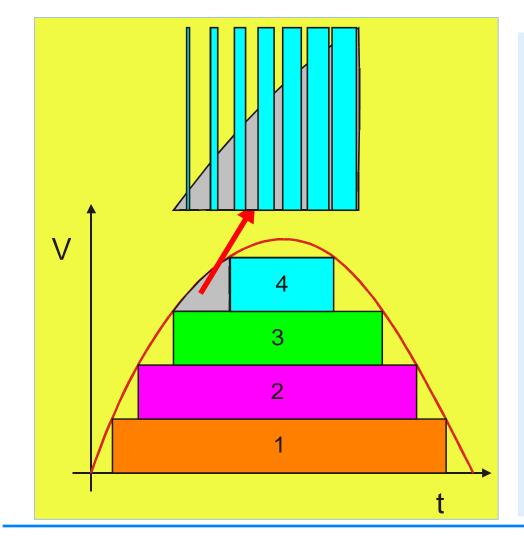

- For accurate voltage control a PWM is superimposed on the switching control
- To eliminate the PWM frequencies, a lowpass filter has to be used in the output circuit
- In this way, PWM allows very accurate voltage regulation




# **Module Rotation**

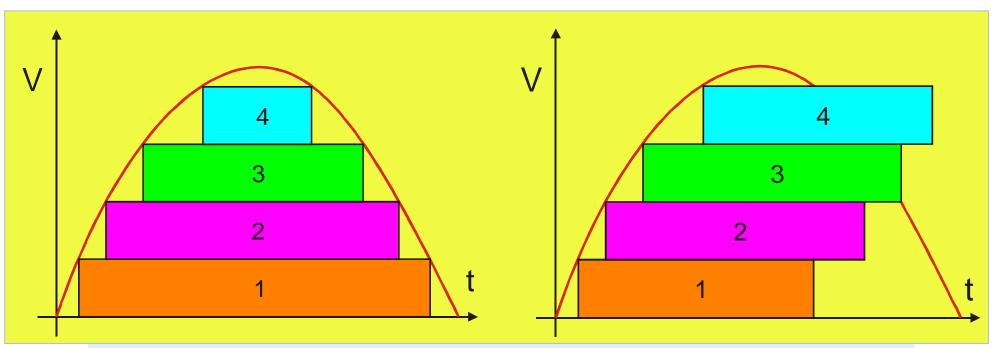

- The modules are controlled such that:
  - The module switched on the longest time is switched off next (FIFO)
  - The module switched off the longest time is switched on next (FIFO)
- Resulting in equal loading for all modules


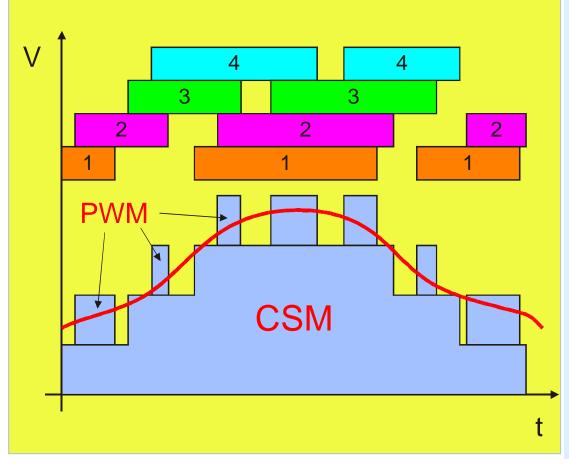
# Combination of PWM / CSM and Module Rotation




The final control algorithm achieves:

- Equal loading of all modules
  - Lower switching frequency allows high PWM frequency small switching losses
  - Small filter requirements
    Drastic reduction of PWM
    voltage and stored energy
    High PWM frequency
    reduces the required filter
    size



# **System Block Diagram**

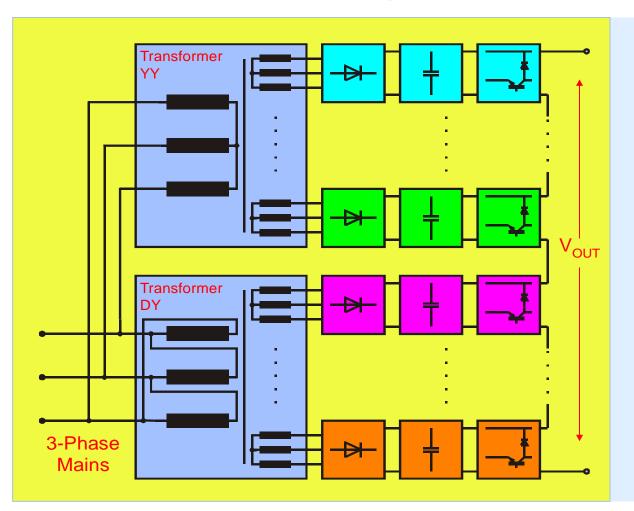

Each Module is supplied from a separate secondary winding of a mains transformer


- Provides Voltage Insulation between the modules
- Transformer is available either with air, cast resin or oil insulation
- Available for mains voltages from 400V to 30 kV

Two different transformers with different phase shifts are used

- 12-pulse rectification
- high power factor of > 0.95



# **Power Module**

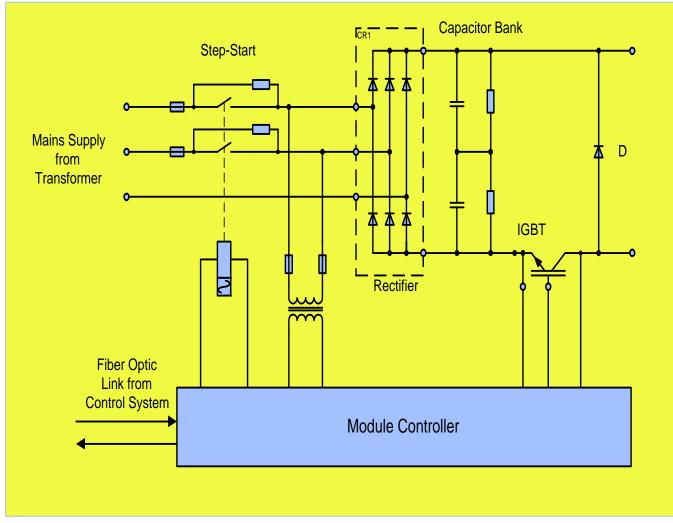


- Modern IGBT switching devices
- Integrated stepstart-system
- Controlled by the PSM control system via fiber optic link
- Integrated safety features

   Short-Circuit protection
   IGBT supervision





# **Module for PSI application**

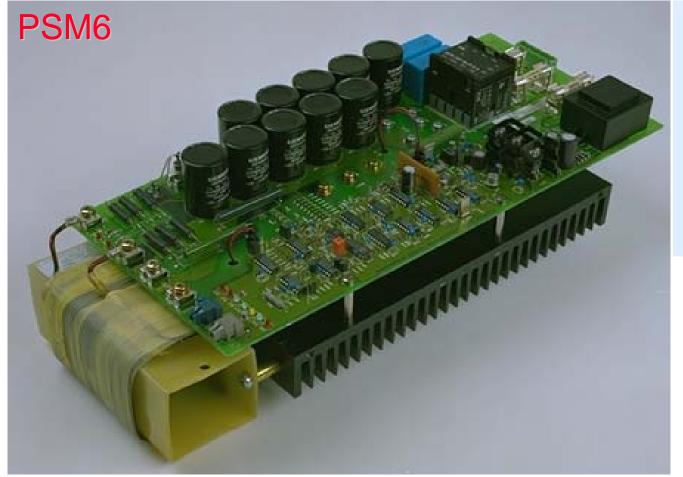

#### **PSM 6 Module**

- Air Cooled
- 25 A peak current
- 700 V output level



# **PSM for Scientific Applications**



Paul Scherrer Institut, 5232 Villigen-PSI, Switzerland

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron



# **HVPS for Scientific Applications 1**

- PSM : the ideal solution for various Scientific Applications
  - Large bandwidth in control system, well suited for pulsed systems
    - No limitation for the maximum pulse length
    - Minimum pulse length ~ 10  $\mu$  s
  - High efficiency, reduced energy costs for DC loads
    - Typical efficiency better than 97%
- Crowbarless operation, even for very sensitive loads
  - Fast switching-off ( < 10 us)
  - Eliminates the need for a crowbar system
  - Typical short circuit energy of less than 5 to 20 J





# **HVPS for Scientific Applications 2**

- Redundancy
  - System remains in operation even with defective modules
  - High reliability and availability
- High power factor of 95% and better due to 12-Pulse rectification
- Fully digital control system, no need for adjustments
- Galvanic separation of control system with fiber optic links
- The first klystron system with PSM was operational since 2000





# PSM @ PSI




Paul Scherrer Institut, 5232 Villigen-PSI, Switzerland

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron






# Layout of SLS

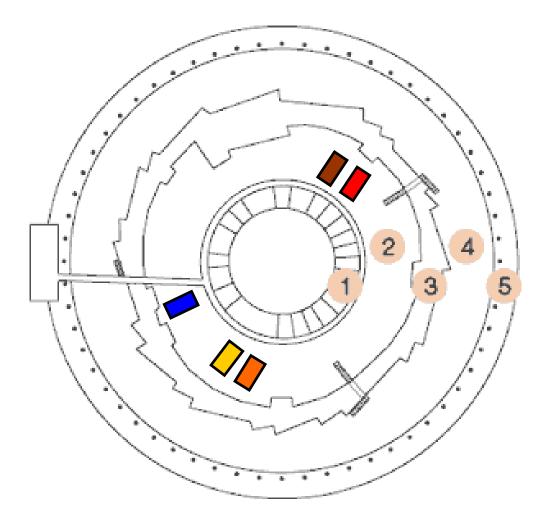


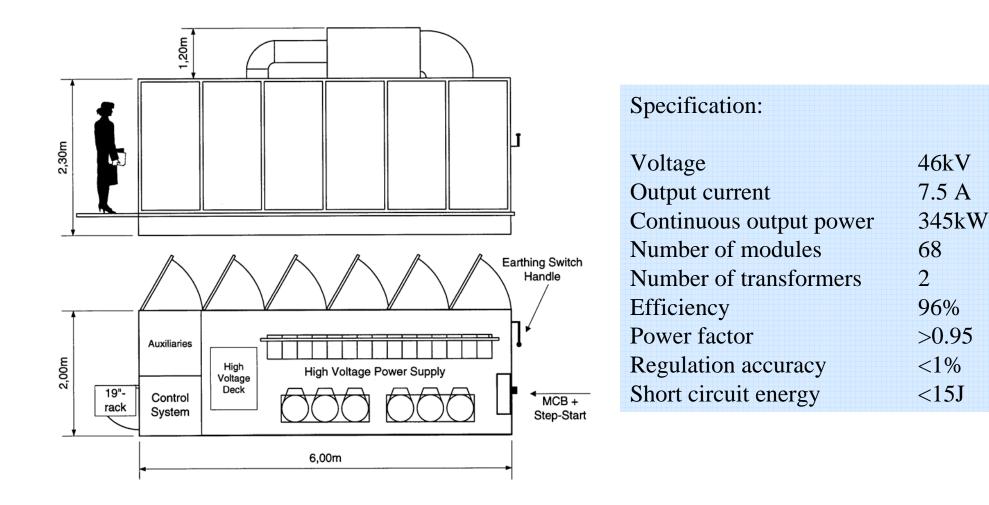
# Layout of PSI High Voltage Power Supply







### Front view of the HVPS





# **Digital and Analog I/O**





# **Control Rack**







### **Back and side view of the HVPS**







### **Access to Modules**







# **PSM Module Support**








### **PSM Transformers and HV-Deck**







# **High Voltage Deck**

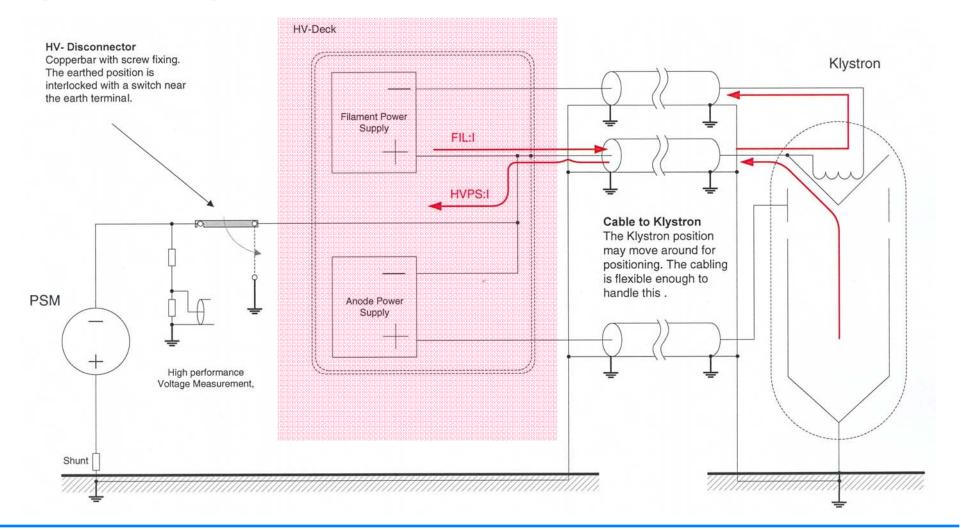

Fourth CW and High Average Power RF Workshop / May 2006 / W. Tron





## **Defective components**

Only 2 components were defective from 340 modules after the first year :

- Control Print

- Resistor in Step Start Circuit



## Acknowledgement

I would like to thank

Thomson Broadcast & Multimedia AG Juergen Alex (Juergen.Alex@thomson-bm.ch) Spinnereistrasse 5300 Turgi / Switzerland Phone +41 56 299 2455 Fax +41 56 223 5051

For their contribution to this presentation.